

Question Paper

Paper-II

Q-1) A) Select correct alternative and rewrite the sentence. (4)

1) For use as an amplifier, the transistor must be operated in ----- region.

i) Saturation ii) active iii) cut off iv) upper

2) At absolute temperature ,an intrinsic semiconductor has -----

i) A few electrons ii) many holes iii) many free electrons iv) no free electrons or no holes

3) If the PIV rating of a diode is exceeded, -----.

i) The diode conducts poorly ii) the diode behaves as Zener diode
iii) the diode is destroyed iv) the diode work as capacitor

4) .A transistors converts -----

i) Dc power into ac power ii) ac power into dc power iii) high resistance into low resistance iv) low resistance into high resistance

Q-1)B) Answer any two of the following questions. (6)

1) Write a note on intrinsic semiconductor.

2) Explain operation of NPN transistor.

3) What do you mean by biasing? Explain the need for bias stabilisation

Q-2) A) Answer any two of the following questions. (6)

1) Define: i) depletion layer, ii) barrier potential iii) knee voltage.

2) Calculate I_E in a transistor for which $\beta=50$ and $I_B=20\mu A$.

3) Write a note fixed bias.

Q.2) B) Answer any one of the following question. (4)

- 1) Define α and β of transistor? Obtain the relation between α and β .
- 2) Define the behaviour of a PN junction under forward and reverse

Q-3) A) Answer any two of the following questions. (6)

- 1) Compare :conductors ,semiconductors ,and insulators
- 2) In a common base connection, $I_E=1\text{mA}$, $I_C=0.95\text{mA}$ calculate the value of I_B .
- 3) Explain the use of transistor as switch.

Q-3) B) Answer any one of the following. (4)

- 1) Calculate the co-ordinates of operating point if fixed bias method is used and $R_c = 1.2\text{ k}\Omega$, $R_B=100\text{k}\Omega$ and $V_{CC} = 8\text{V}$ and $\beta = 50$.
- 2) Calculate the value of I_B I_C and I_E in collector to base biasing method. $V_{CC}=9\text{V}$, $R_B = 1\text{m}\Omega$, $R_c = 3\Omega$ and $\beta = 95$ and $R_E = 1\text{k}\Omega$.

Q-4) A) Answer any two of the following questions. (6)

- 1) Explain V-I characteristics of P-N junction diode .Draw the circuit diagram .
- 2) What do you mean by amplifier ? Explain common base transistor configuration .
- 3) Compare BJT and FET

Q-4) B) Answer any one of the following. (4)

- 1) Explain collector to base bias circuit.
- 2) Explain decibel gain of multistage amplifier.Why dB scale is used in amplifiers.

Q-5) A) Answer any two of the following. (6)

- 1) Write a note on p-type semiconductor .
- 2) Explain the construction of a junction transistor and draw the symbols.
- 3) Explain collector to base bias circuit

Q-5) B) Answer any one of the following. (4)

- 1) Draw circuit diagram of typical common emitter amplifier and explain the function of each component in it.
- 2) Write the classification of amplifiers.

OR

Q-5) A) Answer any two of the following. (6)

- 1) Write a note on N-type semiconductor
- 2) Explain doping and areas of emitter base and collector regions in a transistor.
- 3) Explain voltage divider biasing circuit.

B) Answer any one of the following. (4)

- 1) In a transistor circuit if $V_{cc}=10\text{ v}$, $R_c=5\text{K}$ zero signal base current $25\mu\text{A}$ and $\beta=40$. Find the co-ordinates of load line and operating point. Draw loadline.
- 2) Draw circuit diagrams for three configurations of a transistors.